

Student's name \_\_\_\_\_

Discussion section # \_\_\_\_\_

(Last, First, write legibly, use ink)

(use ink)

Instructor is **not responsible** for grading and entering scores for HW papers lacking clear information in the required fields above

### Problem 1 (30 points) Summing Amplifier, or Adder; Application for sensor circuits

In all parts of this problem, use the "Golden Rules"

#### Part 1 (10 points)



Use the node voltage equation for node A to express the output voltage as the sum of two amplified input voltages in the form:

$$V_{OUT} = V_{S1} \cdot \text{Gain}_1 + V_{S2} \cdot \text{Gain}_2 \quad [\text{equation 1}]$$

Express the gain values in terms of the resistances  $R_F$ ,  $R_1$  and  $R_2$ ; pay attention to the signs. **Show your work on a separate page.** Your answers:

$$\text{Gain}_1 = -\frac{R_f}{R_1}$$

$$\text{Gain}_2 = -\frac{R_f}{R_2}$$

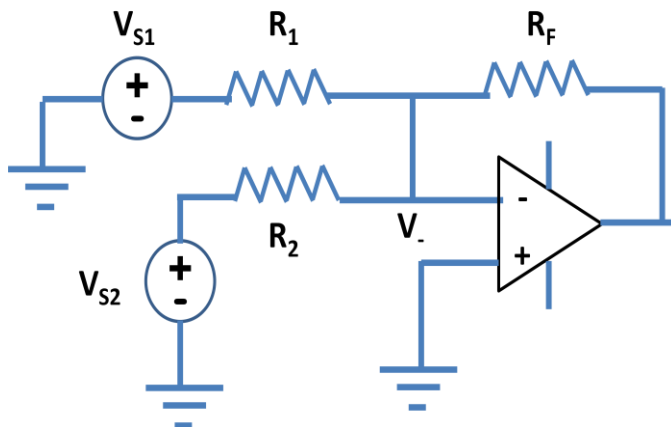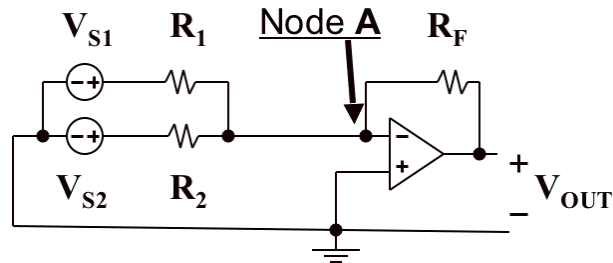

The node voltage equation for the above circuit is

$$\frac{V_- - V_{S1}}{R_1} + \frac{V_- - V_{S2}}{R_2} - \frac{V_- - V_{out}}{R_F} = 0$$

Using the golden rule we have

$$V_{out} = V_{S1} \times -\frac{R_f}{R_1} + V_{S2} \times -\frac{R_f}{R_2}$$

$$\text{Gain}_1 = -\frac{R_f}{R_1}; \text{Gain}_2 = -\frac{R_f}{R_2}$$

Student's name \_\_\_\_\_

Discussion section # \_\_\_\_\_

(Last, First, write legibly, use ink)

(use ink)

Instructor is **not responsible** for grading and entering scores for HW papers lacking clear information in the required fields above

## Part 2 (20 points) Practical Perspective

The pressure sensor for your project has the zero offset equal to 0.25 V and the sensitivity equal to 0.15 V/psi. (See the file "Pressure sensor specs" for more detail.) Thus, at 5 psi the sensor's output equals:

$$V_{S1, 5 \text{ psi}} = (0.25 \text{ V}) + (5 \text{ psi}) \frac{0.15 \text{ V}}{\text{psi}} = 1.00 \text{ V}$$

**You need the  $V_{OUT}$  readings: exactly 0 V at 5 psi and exactly 10 V at 10 psi.**

To achieve this goal, use an adder circuit with two sources – the pressure sensor as  $V_{S1}$  and a 1.5 V battery as  $V_{S2}$ . Use  $R_F = 100 \text{ k}\Omega$ . Calculate the input resistances  $R_1$  and  $R_2$  in  $\text{k}\Omega$ . **Show your work on a separate page.** Your answers:

$$R_1 = \underline{7.5} \text{ k}\Omega \quad R_2 = \underline{11.25} \text{ k}\Omega$$

### Hints:

1. Algebraically, you have to write [equation 1] twice: for the output at 5 psi and for the output at 10 psi, thus obtain two equations with two unknown resistances  $R_1$  and  $R_2$ ; then solve for  $R_1$  and  $R_2$ .
2. To match the desired polarity of the output voltage, you can connect the sensor and/or the battery in any of the two ways; for example, at 5 psi, you can obtain either  $V_{S1} = +1 \text{ V}$  or  $V_{S1} = -1 \text{ V}$ . Keep the chosen connection at all pressures. **Clearly explain which connection you choose.**

Using the equation derived in the part 1 of the problem

$$V_{out} = V_{S1} \times -\frac{R_f}{R_1} + V_{S2} \times -\frac{R_f}{R_2}$$

Here  $R_f = 100 \text{ k}\Omega$  and  $V_{S2} = 1.5 \text{ V}$  and  $R_1$  and  $R_2$  are in  $\text{k}\Omega$

The value of  $V_{S1}$  at 5 psi is  $0.25 + 0.15 \times 5 = 1.0 \text{ V}$

$V_{S1}$  at 10 psi is  $0.25 + 0.15 \times 10 = 1.75 \text{ V}$

Here the objective is to achieve a positive output voltage. In the inverting configuration we have to connect both the voltages sources in the reverse way as shown in the diagram.


Student's name \_\_\_\_\_

Discussion section # \_\_\_\_\_

(Last, First, write legibly, use ink)

(use ink)

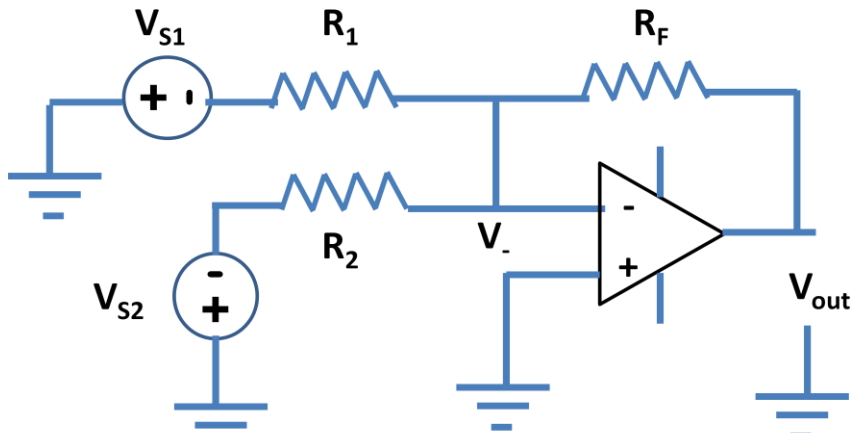Instructor is **not responsible** for grading and entering scores for HW papers lacking clear information in the required fields above



From the node voltage equations we obtain

$$1 \times \frac{100}{R_1} + 1.5 \times \frac{100}{R_2} = 0; \quad (\text{eqn. 1})$$

$$1.75 \times \frac{100}{R_1} + 1.5 \times \frac{100}{R_2} = 10; \quad (\text{eqn. 2})$$

Upon solving these equations we get

$$R_1 = 7.5 \text{ k}\Omega \text{ and } R_2 = 11.25 \text{ k}\Omega.$$

Student's name \_\_\_\_\_

Discussion section # \_\_\_\_\_

(Last, First, write legibly, use ink)

(use ink)


Instructor is **not responsible** for grading and entering scores for HW papers lacking clear information in the required fields above

## Problem 2 (30 points) Integrator and Differentiator based on Op Amps; Prototype of PID control circuit


In both parts, apply the "Golden Rules"

### Part 1 (10 points)

#### Integrator

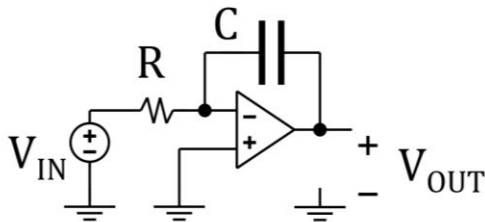

#### Differentiator

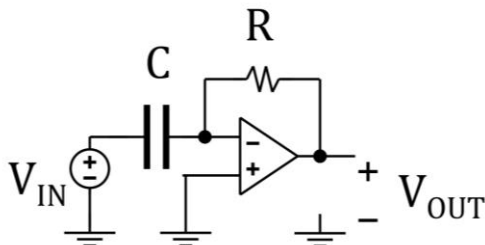






Which of the sketches 1-4 most likely represents the input voltage? Your answers:

For the Integrator: 1

For the Differentiator: 4

An alternative is: *None of the above.*

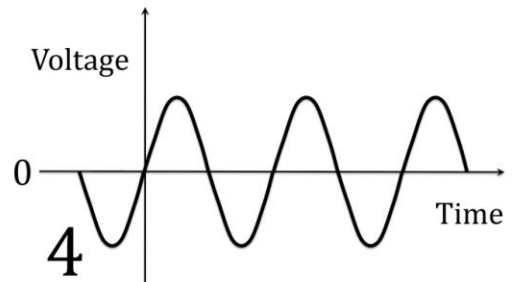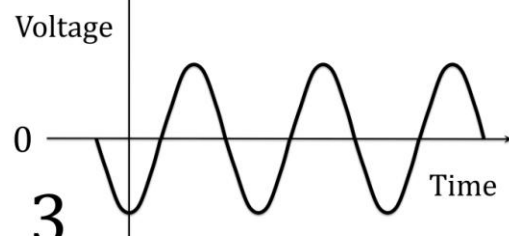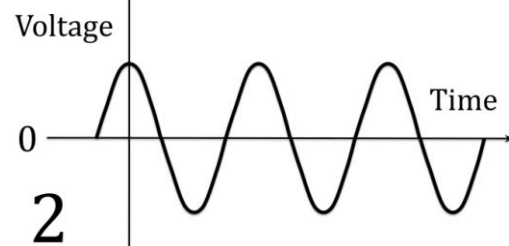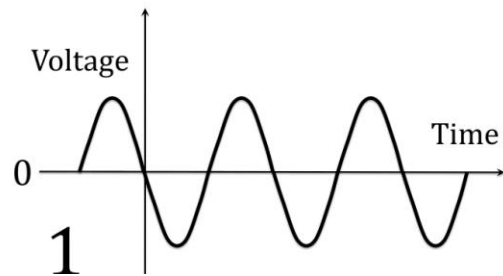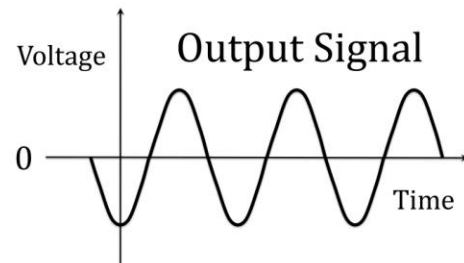**On a separate page, show your work: use equations to justify your answers.**



Student's name \_\_\_\_\_

Discussion section # \_\_\_\_\_

(Last, First, write legibly, use ink)

(use ink)

Instructor is **not responsible** for grading and entering scores for HW papers lacking clear information in the required fields above

The output signal can be represented as a sinusoidal wave of the form

$$V_{out} = A \sin(\omega t - \pi/2) = -A_1 \cos(\omega t)$$

The inverting integrator integrates a input function and the resulting wave will be

$$V_{out} = -\frac{1}{RC} \int V_{in}(t) dt$$

Therefore

$$V_{in} = -A_2 \sin(\omega t)$$

This waveform is similar to #1

For an inverting differentiator we have

$$V_{out} = -RC \frac{dV}{dt}$$

$$V_{in} = A_3 \sin(\omega t)$$

This waveform is similar to #4

Student's name \_\_\_\_\_

Discussion section # \_\_\_\_\_

(Last, First, write legibly, use ink)

(use ink)

Instructor is **not responsible** for grading and entering scores for HW papers lacking clear information in the required fields above

## Problem 2

### Part 2 (20 points)

A control system measures the error, or difference between the set point and the actual output of the Plant (the device to be controlled).


In PID (Proportional, Integral, and Differential) control system, the error is amplified (triangular symbol on the diagram), integrated, and differentiated;

the sum of all three parts is

further amplified and fed into an actuator (such as motor, heater, cooler, lighting, etc.) that takes action on the Plant. The output of a sensor installed in the Plant is fed back to the input of the control system.

All components of such system can be implemented with Op Amps. The necessary blocks include: Integrator and Differentiator, Amplifiers (Inverting, Non-Inverting, and Difference), and the Buffer, or Voltage Follower: see the diagrams below.

### PID Control System

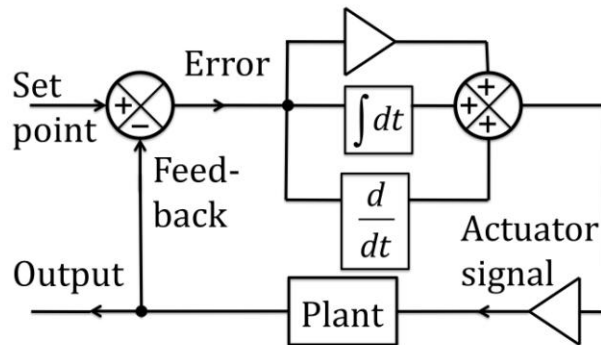


© 2010 A. Ganago


Op Amp Blocks

12

### Buffer, or Voltage Follower

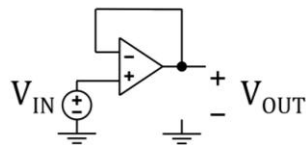

### Inverting Amplifier

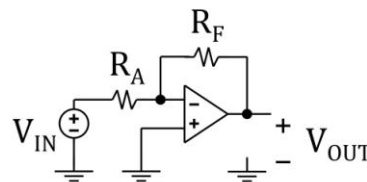

Student's name \_\_\_\_\_


Discussion section # \_\_\_\_\_

(Last, First, write legibly, use ink)


(use ink)

Instructor is **not responsible** for grading and entering scores for HW papers lacking clear information in the required fields above

## Inverting Adder, or Summer

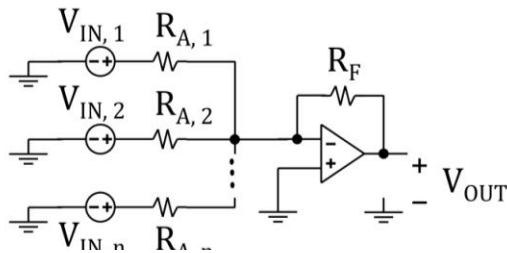

## Non-Inverting Amplifier

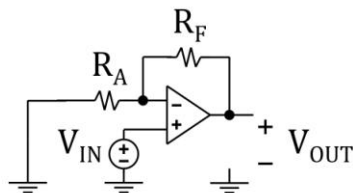

## Problem 2 Part 2, continued

The output of the Difference Amplifier shown on this diagram equals:

$$V_{OUT} = (V_{IN,1} - V_{IN,2}) \frac{R_F}{R_A}$$


Consider the prototype of a PID control circuit shown below.

Assume that the Actuator signal should be:

$$\text{Actuator Signal} = \left[ 0.5 \cdot (\text{Error}) + \frac{d}{dt}(\text{Error}) + \int (\text{Error}) dt \right]$$

where *Error* is the output of the Difference Amplifier. For simplicity, assume  $R \cdot C = 1$ .

## Difference Amplifier

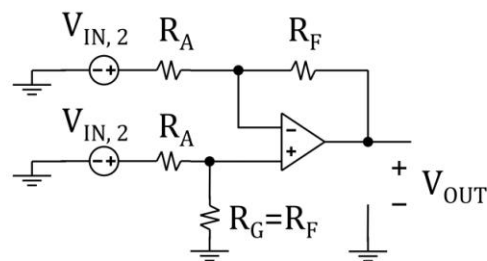

Student's name \_\_\_\_\_


Discussion section # \_\_\_\_\_

(Last, First, write legibly, use ink)

(use ink)

Instructor is **not responsible** for grading and entering scores for HW papers lacking clear information in the required fields above
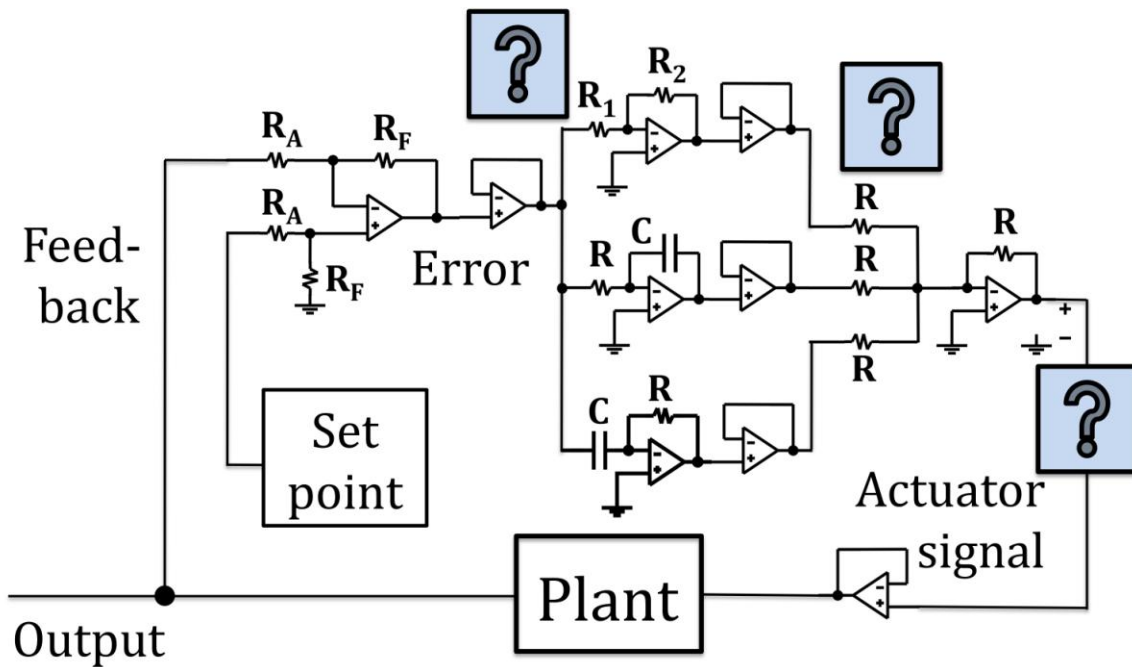
## Questions on Prototype Control Circuit



© 2010 A. Ganago

Op Amp Blocks

14

Answer the following questions:



Student's name \_\_\_\_\_

Discussion section # \_\_\_\_\_

(Last, First, write legibly, use ink)

(use ink)

Instructor is **not responsible** for grading and entering scores for HW papers lacking clear information in the required fields above

## Problem 2 Part 2, continued

1. Given  $R_2 = 100 \text{ k}\Omega$ , determine  $R_1$  in  $\text{k}\Omega$ .

Your answer:  $R_1 = \underline{200} \text{ k}\Omega$ .

From the actuator signal relation we see that the proportional part of the PID controller has a factor of 0.5. This can be achieved only when the gain of the inverting amplifier that is part of the P section has a gain of 0.5.

Gain =  $-R_2/R_1 = 0.5$ ; therefore  $R_1 = 200 \text{ k}\Omega$ .

2. Note that the diagram includes an inverting amplifier for the error signal.

Is an additional inverting amplifier needed before the adder?

Your answer: Yes ☒ No (circle one)

If you answered Yes, calculate  $R_1$  in  $\text{k}\Omega$  for the additional inverting amplifier (assume  $R_2 = 100 \text{ k}\Omega$ , as above).

Your answer:  $R_1 = \underline{NA} \text{ k}\Omega$ .

Inverter is not necessary here. The polarity of the signal output from the voltage follower stages is negative. This results in the adder output voltage being positive. The input or the outcome does not in any way affect the functionality of the circuit.

3. Is an additional inverting amplifier needed after the adder?

Your answer: Yes ☒ No (circle one)

If you answered Yes, calculate  $R_1$  in  $\text{k}\Omega$  for the additional inverting amplifier (assume  $R_2 = 100 \text{ k}\Omega$ , as above).

Your answer:  $R_1 = \underline{N/A} \text{ k}\Omega$ .

Justify your answers. Show your work below and/or on additional pages.

The signal input from the PID section has to be subtracted from the setpoint value in order to get the error. Thus an inverter is not required as the difference amplifier stage requires positive voltage inputs in order to function as a subtractor.

### Comment.

An inverter with  $R_1 = R_2$  multiplies the signal by  $(-1)$ ; thus putting two inverters in series produces multiplication by  $(-1) \cdot (-1) = +1$ , which is unnecessary. Your design should avoid unnecessary inverters.

Student's name \_\_\_\_\_

Discussion section # \_\_\_\_\_

(Last, First, write legibly, use ink)

(use ink)

Instructor is **not responsible** for grading and entering scores for HW papers lacking clear information in the required fields above

### Problem 3 (30 points) Active filters based on Op Amps

In both parts, apply the "Golden Rules"

#### Part 1 (10 points)


Determine the type of filter (LP, HP, BP, or BR) for the circuit shown here.

Your answer: **High-Pass**


Show your work on a separate page:

- (A) Redraw the circuit at a very low frequency  $\omega \rightarrow 0$  and at a very high frequency  $\omega \rightarrow \infty$

Small  $\omega$

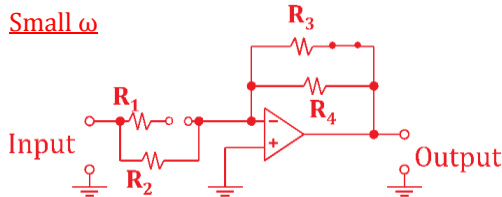

Large  $\omega$

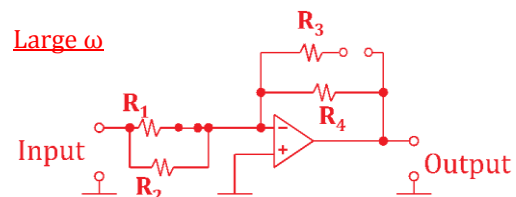

- (B) On each redrawn circuit, show the capacitor and inductor as an open/closed switch

*With small  $\omega$ , inductors act as short circuits, and capacitors act as open circuits.*

*With large  $\omega$ , inductors act as open circuits, and capacitors act as short circuits.*

- (C) Write the algebraic expression for the transfer function magnitude at  $\omega \rightarrow 0$  and at  $\omega \rightarrow \infty$

Small  $\omega$

*This is an inverting op-amp with  $R_f = R_3 \parallel R_4$  and  $R_i = R_2$ . Thus, the transfer function is*


$$\frac{R_3 R_4}{R_3 + R_4} * \frac{1}{R_2} = \frac{R_3 R_4}{R_2 (R_3 + R_4)}$$

Large  $\omega$

*This is an inverting op-amp with  $R_f = R_4$  and  $R_i = R_2 \parallel R_1$ . Thus, the transfer function is*

$$R_4 * \frac{R_1 + R_2}{R_1 R_2} = \frac{R_4 (R_1 + R_2)}{R_1 R_2}$$

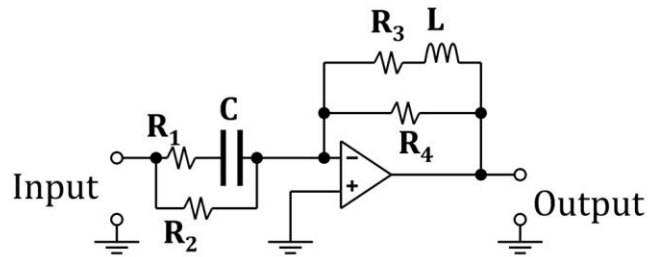*We see that a  $R_4/R_2$  is present in each term. Because  $R_3/(R_3+R_4) < 1$  and  $(R_1+R_2)/R_1 > 1$ , the transfer function is larger for large  $\omega$ . As a result, we are working with a high-pass filter.*




Student's name \_\_\_\_\_

(Last, First, write leg

Instructor is **not responsible** for g  
clear informati

## Problem 3

## Part 2 (20 points)

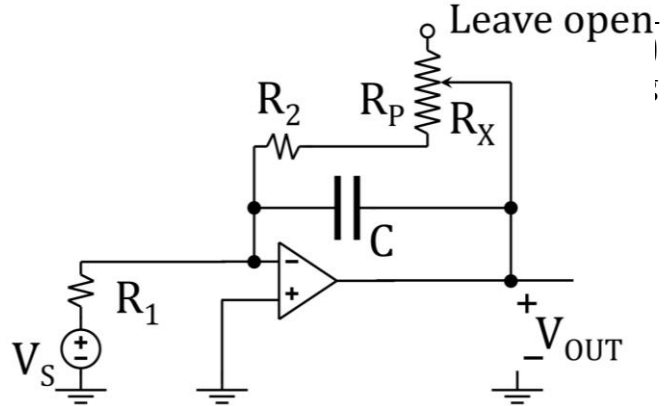For the circuit shown here, do  
the following:

- (A) Determine the type of
- 
- filter. Your answer:

**Low-Pass**

- (B) Derive the algebraic expression for the transfer function
- $H(\omega) = \frac{V_{OUT}(\omega)}{V_S(\omega)}$
- .

$$H(j\omega) = -\frac{R_f}{R_i} = -\frac{(R_2 + R_X) \parallel C}{R_1} = -\frac{(R_2 + R_X) \frac{1}{j\omega C}}{R_1(R_2 + R_X + \frac{1}{j\omega C})} = -\frac{R_2 + R_X}{R_1 + j\omega C R_1(R_2 + R_X)}$$

- (C) Derive the algebraic expression for the cutoff frequency
- $\omega_c$

$$\begin{aligned} \frac{\max(|H(j\omega)|)}{\sqrt{2}} &= \frac{R_2 + R_X}{R_1 \sqrt{2}} = |H(j\omega_c)| = \frac{R_2 + R_X}{\sqrt{R_1^2 + \omega_c^2 C^2 R_1^2 (R_2 + R_X)^2}} \\ \frac{1}{\sqrt{2}} &= \frac{1}{\sqrt{1 + \omega_c^2 C^2 (R_2 + R_X)^2}} \\ 1 + \omega_c^2 C^2 (R_2 + R_X)^2 &= 2 \\ \omega_c &= \frac{1}{C(R_2 + R_X)} \end{aligned}$$

- (C) Derive the algebraic expression for zero-frequency gain for any value of
- $R_X$

$$|H(\omega=0)| = \left| \frac{V_{OUT}(\omega=0)}{V_S(\omega=0)} \right| \quad \text{When } \omega=0, \text{ the imaginary term of the denominator drops out.}$$

Your answer:  $\frac{R_2 + R_X}{R_1}$ 

- (D) Derive the algebraic expression for the product of zero-frequency gain and the cutoff frequency
- $\omega_c$
- (called the "Gain · Bandwidth" product) for any value of
- $R_X$

Your answer:

$$\frac{1}{C(R_2 + R_X)} * \frac{R_2 + R_X}{R_1} = \frac{1}{C R_1}$$

Does it depend on the value of  $R_X$ ? Yes **No** (circle one)

- (E) Use the following circuit parameters:
- $R_1 = R_2 = 1 \text{ k}\Omega$
- ;
- $R_P = 100 \text{ k}\Omega$
- ;
- $C = 100 \text{ nF}$
- .
- 
- Given that
- $V_S$
- is a sine wave at 100 mV peak amplitude, calculate the peak

Student's name \_\_\_\_\_

Discussion section # \_\_\_\_\_

(Last, First, write legibly, use ink)

(use ink)

Instructor is **not responsible** for grading and entering scores for HW papers lacking clear information in the required fields above

amplitude of the output sine wave at the maximal and minimal values of  $R_X$  for two frequencies: 200 Hz and 5 kHz. Compare with the circuit, from which the capacitor is disconnected. Write the results in the table below:

Input signal frequency	Peak amplitude (in volts) of the output in the given circuit		Peak amplitude (in volts) of the output in the circuit without C	
	$R_X = 0$	$R_X = R_P$	$R_X = 0$	$R_X = R_P$
200 Hz	<b>99.2 mV</b>	<b>793 mV</b>	<b>100 mV</b>	<b>10.1 V</b>
5 kHz	<b>30.3 mV</b>	<b>31.8 mV</b>	<b>100 mV</b>	<b>10.1 V</b>

**On a separate page, show your work for all parts of this problem.**

- Row 1, Column 1:

$$|H(j2\pi * 200)| = \left| \frac{1000 + 0}{1000 + j(2\pi * 200)(100 * 10^{-9})(1000)(1000 + 0)} \right| = 0.992$$

$$\text{Peak output} = |H(\omega)| * V_{IN} = 0.992 * 100 \text{ mV} = \underline{\underline{99.2 \text{ mV}}}$$

- Row 1, Column 2:

$$|H(j2\pi * 200)| = \left| \frac{1000 + 100 * 10^3}{1000 + j(2\pi * 200)(100 * 10^{-9})(1000)(1000 + 100 * 10^3)} \right| = 7.93$$

$$\text{Peak output} = |H(\omega)| * V_{IN} = 7.93 * 100 \text{ mV} = \underline{\underline{793 \text{ mV}}}$$

- Row 1, Column 3:

$$|H(j2\pi * 200)| = \left| \frac{1000}{1000} \right| = 1.00$$

$$\text{Peak output} = |H(\omega)| * V_{IN} = 1.00 * 100 \text{ mV} = \underline{\underline{100 \text{ mV}}}$$

- Row 1, Column 4:

$$|H(j2\pi * 200)| = \left| \frac{1000 + 100 * 10^3}{1000} \right| = 101$$

$$\text{Peak output} = |H(\omega)| * V_{IN} = 101 * 100 \text{ mV} = \underline{\underline{10.1 \text{ V}}}$$

- Row 2, Column 1:

$$|H(j2\pi * 5000)| = \left| \frac{1000 + 0}{1000 + j(2\pi * 5000)(100 * 10^{-9})(1000)(1000 + 0)} \right| = 0.303$$

$$\text{Peak output} = |H(\omega)| * V_{IN} = 0.303 * 100 \text{ mV} = \underline{\underline{30.3 \text{ mV}}}$$

- Repeat this pattern for the last three entries.

Student's name \_\_\_\_\_

Discussion section # \_\_\_\_\_

(Last, First, write legibly, use ink)

(use ink)


Instructor is **not responsible** for grading and entering scores for HW papers lacking clear information in the required fields above

### Problem 4 (30 points) Control circuits with Comparator, MOSFET, and the Wheatstone bridge: Position sensor

#### Part 1 (10 points)
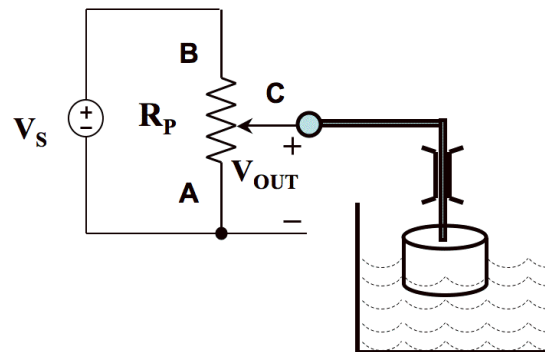
#### Potentiometer as a sensor for linear displacement

The linear potentiometer used is used to measure the amount of liquid in a cylindrical tank. This is similar to how your fuel gage measures how much gas you have in the tank of your car.



Assume the following parameters: the cross-section area of the tank equals  $S = 800 \text{ cm}^2$ ; the length of the linear potentiometer (from A to B) equals  $L = 12 \text{ cm}$ ; the middle position of the potentiometer's tap corresponds to the liquid level equal to  $H = 7 \text{ cm}$ ; the total resistance of the potentiometer is  $R_P = 240 \text{ k}\Omega$ ; the source voltage is  $V_S = 14 \text{ V}$ .

Evidently, the circuit's readings are accurate only if the volume of liquid in the tank  $P$  remains within certain limits: if the float moves too low, the output voltage equals zero regardless of the amount of liquid; if the float moves too high, the output voltage saturates at  $V_S$  regardless of the amount of liquid.

Obtain and record the algebraic expressions for  $P_{\text{MIN}}$  and  $P_{\text{MAX}}$  in terms of  $S$ ,  $L$ , and  $H$ . Neglect the volume of the float.

Your answers:  $P_{\text{MIN}} = S(H - \frac{L}{2})$      $P_{\text{MAX}} = S(H + \frac{L}{2})$

Calculate and record below the minimal and maximal volumes of liquid in the tank  $P_{\text{MIN}}$  and  $P_{\text{MAX}}$  in liters (1 liter = 1,000  $\text{cm}^3$ ) that can be accurately measured with this circuit.

Your answers:  $P_{\text{MIN}} = \mathbf{0.8 \text{ L}}$      $P_{\text{MAX}} = \mathbf{10.4 \text{ L}}$

Show your work below and/or on additional pages.

*Volume = Surface Area · Depth, so we just need to find the minimum and maximum depths. We know that  $H = 7\text{cm}$  corresponds to the center point of the potentiometer,  $6\text{cm}$ . Thus, the minimum potentiometer position will occur at  $H - L/2 = 1\text{cm}$ , and the maximum will occur at  $H + L/2 = 13\text{cm}$ .  $P_{\text{MIN}} = 800\text{cm}^2 \cdot 1\text{cm} = 800\text{cm}^3 = 0.8\text{L}$ .  $P_{\text{MAX}} = 800\text{cm}^2 \cdot 13\text{cm} = 10400\text{cm}^3 = 10.4\text{L}$ .*

Student's name \_\_\_\_\_

Discussion section # \_\_\_\_\_

(Last, First, write legibly, use ink)

(use ink)


Instructor is **not responsible** for grading and entering scores for HW papers lacking clear information in the required fields above

### Problem 4

#### Part 2 (10 points)
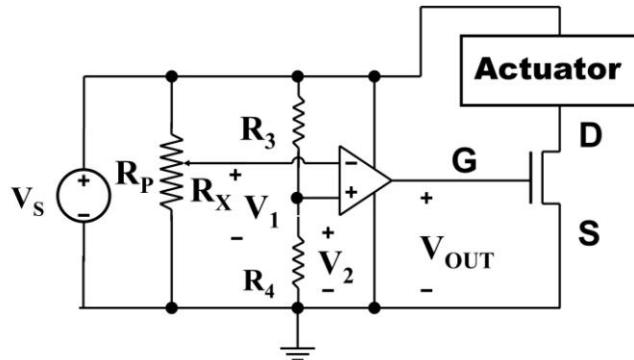
##### Operation of the control circuit

Assume that the potentiometer as the liquid level sensor, which you studied in Part 1 of this problem, is connected to the circuit shown here:  $R_X$  is the resistance between A and B; voltage  $V_{OUT}$  of the diagram in Part 1 is labeled  $V_1$  on the diagram in Part 2.



Position sensor based on potentiometer

**The circuit must keep the level of liquid in the tank below the safe limit.**

Determine what kind of Actuator should be used:

- a) Pump that adds liquid to the tank, or
- b) Valve that blocks the flow of liquid into the tank.

Your answer: a b (circle one)

On a separate page, explain how the circuit operates and justify your answer.

*In this circuit, the op-amp acts as a comparator. When the water is low,  $R_X$  is also low. As a result,  $V_1 > V_2$ , meaning that  $V_{OUT} = V_{OUT, MAX}$  and the actuator is turned on. We want to fill the tank, so the "on" state of the actuator should correspond to when a pump is pumping liquid into the tank. When the water reaches the safe limit,  $R_X$  will be larger and we have  $V_1 < V_2$ . As a result, the pump will turn off, and the water in the tank will remain safe.*

#### Part 3 (10 points)

Use the circuit parameters and tank sizes given in Part 1 and design the control circuit that limits the amount of liquid in the tank at exactly 10 liters.

Assume that  $R_3 = 20 \text{ k}\Omega$ , calculate  $R_4$  in  $\text{k}\Omega$ .

Your answer:  $R_4 = \underline{460 \text{ k}\Omega}$

$$x = \frac{10 \text{ L}}{0.8 \text{ cm}} = 12.5 \text{ cm} \quad \frac{x-1}{L} = \frac{R_X}{R_P} = \frac{11.5}{12} = 0.958$$

*With voltage division,  $\frac{R_X}{R_P} = \frac{R_3}{R_3 + R_4} = 0.958$ . Knowing  $R_3 = 20 \text{ k}\Omega$ ,  $R_4 = \underline{460 \text{ k}\Omega}$*

Student's name \_\_\_\_\_

Discussion section # \_\_\_\_\_

(Last, First, write legibly, use ink)


(use ink)

Instructor is **not responsible** for grading and entering scores for HW papers lacking clear information in the required fields above

### Problem 5 (30 points) Resistive sensors: Temperature controller circuit; Real sensors' parameters

In all parts, use "Golden Rule" #1.

#### Part 1 (10 points)

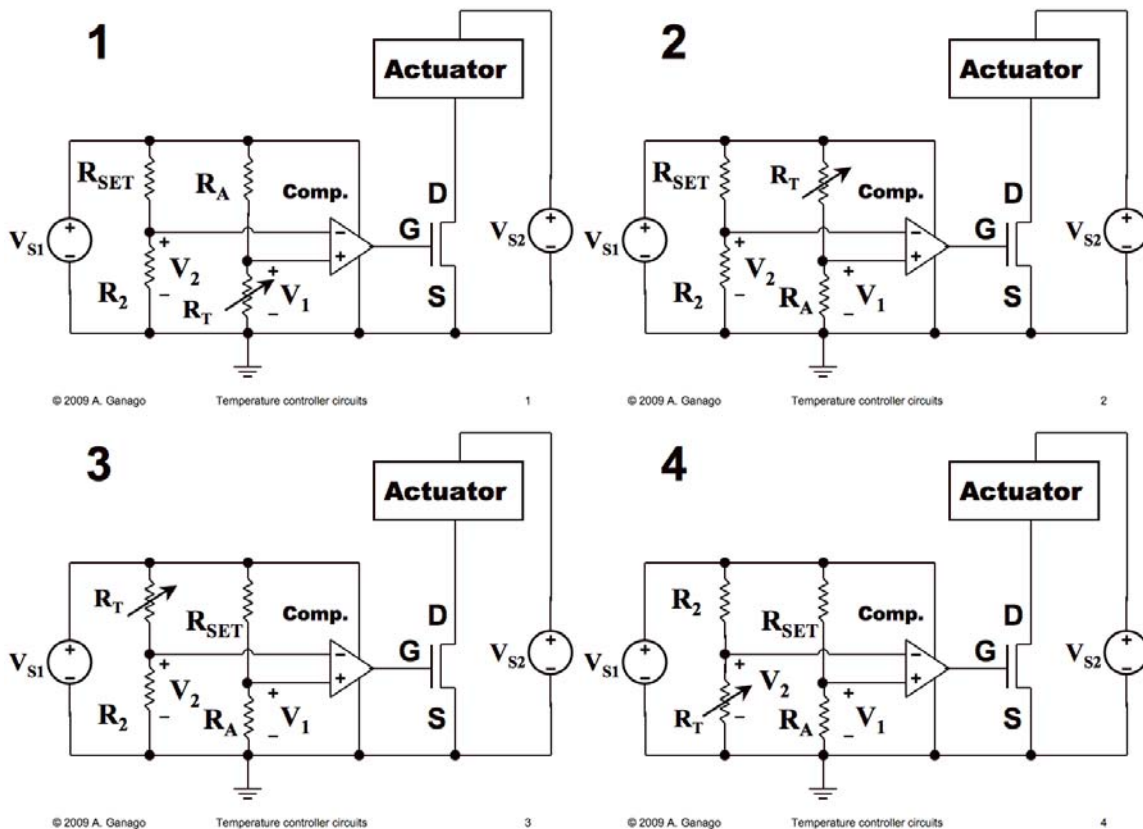

The four circuits shown above are built to maintain the temperature within the desired limits, that is turn on a heater when it gets too cold. We will call the circuit that operates this way a "good" one.

Two types of sensors can be used as  $R_T$ :

- Thermistor with Negative Temperature Coefficient (NTC), and
- Temperature-Dependent Resistor (TDR) with Positive Temperature Coefficient (PTC).

For each of type of sensor, briefly explain (on a separate page) which of the circuits on diagrams 1 – 4 is "good". Explain why each of the "bad" circuits is "bad."

Student's name \_\_\_\_\_

Discussion section # \_\_\_\_\_

(Last, First, write legibly, use ink)

(use ink)

Instructor is **not responsible** for grading and entering scores for HW papers lacking clear information in the required fields above

Notes

- $R_T$  can be PTC or NTC
  - For PTC, as temperature increases resistance increases ( $T \uparrow R \uparrow$ )
  - For NTC, as temperature increases resistance decreases ( $T \uparrow R \downarrow$ )
- Output of comparator goes to  $V_{S1}$  when  $V_+ > V_-$  or  $V_1 > V_2$
- Want heater to be turned on when temperature gets too low
- Heater is turned on when  $V_{GS} > V_T$  of MOSFET, this occurs when output of comparator which equals  $V_{GS}$  goes to  $V_{S1}$
- Heater is on when  $V_+ > V_-$  or  $V_1 > V_2$
- Heater is off when  $V_+ < V_-$  or  $V_1 < V_2$

Circuit 1

$$V_2 = V_{S1} * \frac{R_2}{R_2 + R_{SET}} \quad V_1 = V_{S1} * \frac{R_T}{R_T + R_A}$$

$V_2$  is constant and  $V_1 \uparrow$  as  $R_T \uparrow$


Assume heater off,  $V_1 < V_2$

So as  $T \downarrow$  want  $V_1 \uparrow$  or  $R_T \uparrow$

NTC  $R_T$  would be good choice for this

PTC  $R_T$  would have  $V_1 \downarrow$  as  $T \downarrow$

and heater won't turn on as  $T \downarrow$ , bad choice

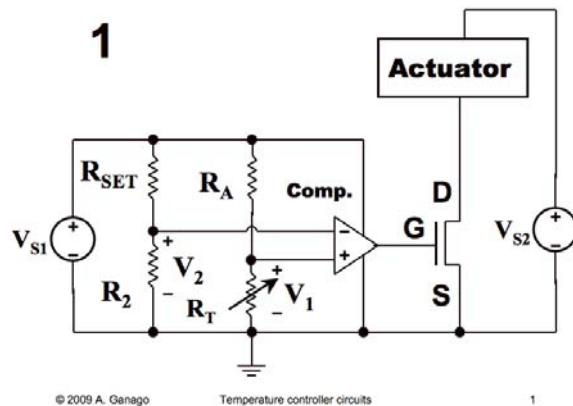Circuit 2

$$V_2 = V_{S1} * \frac{R_2}{R_2 + R_{SET}} \quad V_1 = V_{S1} * \frac{R_A}{R_T + R_A}$$

$V_2$  is constant and  $V_1 \uparrow$  as  $R_T \downarrow$


Assume heater off,  $V_1 < V_2$

So as  $T \downarrow$  want  $V_1 \uparrow$  or  $R_T \downarrow$

PTC  $R_T$  would be good choice for this

NTC  $R_T$  would have  $V_1 \downarrow$  as  $T \downarrow$

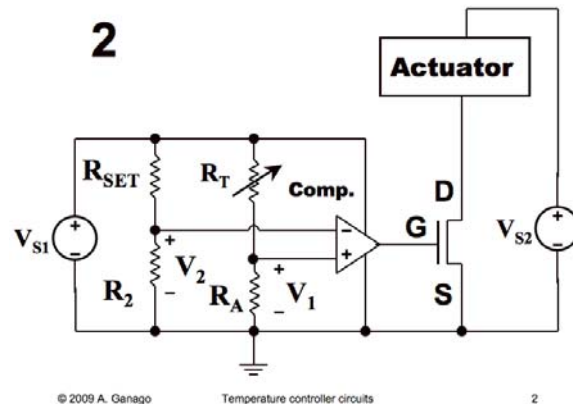and heater won't turn on as  $T \downarrow$ , bad choice





Student's name \_\_\_\_\_

Discussion section # \_\_\_\_\_

(Last, First, write legibly, use ink)

(use ink)

Instructor is **not responsible** for grading and entering scores for HW papers lacking clear information in the required fields above

**Circuit 3**

$$V_2 = V_{S1} * \frac{R_2}{R_2 + R_T} \quad V_1 = V_{S1} * \frac{R_A}{R_{SET} + R_A}$$

$V_1$  is constant and  $V_2 \downarrow$  as  $R_T \uparrow$


Assume heater off,  $V_2 > V_1$

So as  $T \downarrow$  want  $V_2 \downarrow$  or  $R_T \uparrow$

NTC  $R_T$  would be good choice for this

PTC  $R_T$  would have  $V_2 \uparrow$  as  $T \downarrow$

and heater won't turn on as  $T \downarrow$ , bad choice

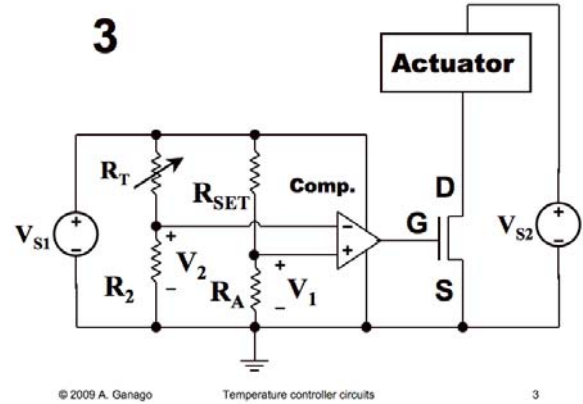**Circuit 4**

$$V_2 = V_{S1} * \frac{R_T}{R_2 + R_T} \quad V_1 = V_{S1} * \frac{R_A}{R_{SET} + R_A}$$

$V_1$  is constant and  $V_2 \downarrow$  as  $R_T \downarrow$


Assume heater off,  $V_2 > V_1$

So as  $T \downarrow$  want  $V_2 \downarrow$  or  $R_T \downarrow$

PTC  $R_T$  would be good choice for this

NTC  $R_T$  would have  $V_2 \uparrow$  as  $T \downarrow$

and heater won't turn on as  $T \downarrow$ , bad choice

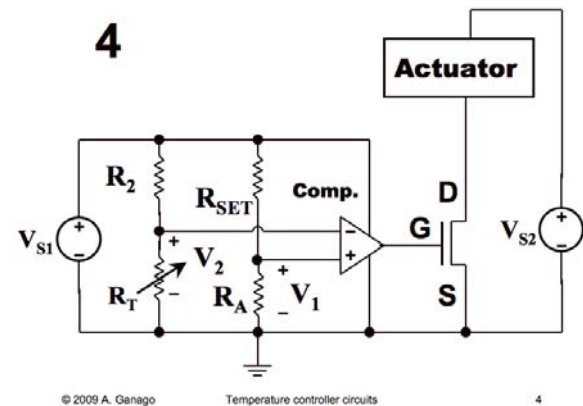**Summary**

	Circuit 1	Circuit 2	Circuit 3	Circuit 4
NTC $R_T$	Good	Bad	Good	Bad
PTC $R_T$	Bad	Good	Bad	Good

Student's name \_\_\_\_\_

Discussion section # \_\_\_\_\_

(Last, First, write legibly, use ink)

(use ink)

Instructor is **not responsible** for grading and entering scores for HW papers lacking clear information in the required fields above

## Problem 5

In Parts 2 and 3, consider the circuits listed below regardless of whether you found them “good” in Part 1.

### Part 2 (10 points)

Consider circuit diagram 3 where  $R_T$  is a thermistor with  $1000\ \Omega$  resistance at  $25\ ^\circ\text{C}$  (see *US Sensor catalog*, page 40, attached),  $R_A = 1\ \text{k}\Omega$ , and  $R_{SET} = 2\ \text{k}\Omega$ . Calculate the resistance  $R_2$  to ensure that the actuator is turned on/off at  $-20\ ^\circ\text{C}$ . Show your work.

Actuator is turned on/off when inputs of comparator are equal or  $V_1 = V_2$

From voltage division,

$$V_2 = V_{S1} \frac{R_2}{R_2 + R_T} \quad V_1 = V_{S1} \frac{R_A}{R_A + R_{SET}}$$

Setting  $V_1 = V_2$  yields:

$$\frac{R_2}{R_2 + R_T} = \frac{R_A}{R_A + R_{SET}}$$

$$\frac{1}{1 + \frac{R_T}{R_2}} = \frac{1}{1 + \frac{R_{SET}}{R_A}}$$

$$\frac{R_T}{R_2} = \frac{R_{SET}}{R_A}$$


$$\frac{R_2}{R_T} = \frac{R_A}{R_{SET}}$$

From the given resistances  $R_A = 1\ \text{k}\Omega$ ,  $R_{SET} = 2\ \text{k}\Omega$ ,

$$\frac{R_2}{R_T} = \frac{R_A}{R_{SET}} = \frac{1\text{k}}{2\text{k}} = \frac{1}{2} \quad R_2 = \frac{1}{2} R_T$$

Looking up thermistor's resistance from table for  $-20^\circ\text{C}$ ,  $R_T = 9708\ \Omega$ . So,
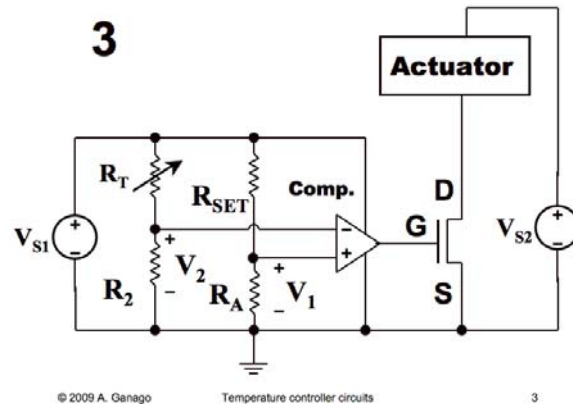
$$R_2 = \frac{1}{2}(9708) = 4854\ \Omega$$



Student's name \_\_\_\_\_

Discussion section # \_\_\_\_\_

(Last, First, write legibly, use ink)

(use ink)

Instructor is **not responsible** for grading and entering scores for HW papers lacking clear information in the required fields above

### Part 3 (10 points)

Consider circuit diagram 4 where  $R_T$  is a TDR with  $1000\ \Omega$  resistance at  $0\ ^\circ\text{C}$  (see *Vishay Beyschlag catalog*, attached),  $R_2 = 2.2\ \text{k}\Omega$ , and  $R_{SET} = 3.3\ \text{k}\Omega$ . Calculate the resistance  $R_A$  to ensure that the actuator is turned on/off at  $-20\ ^\circ\text{C}$ . Show your work.

Actuator is turned on/off when inputs of comparator are equal or  $V_1 = V_2$

From voltage division,

$$V_2 = V_{S1} \frac{R_T}{R_T + R_2} \quad V_1 = V_{S1} \frac{R_A}{R_A + R_{SET}}$$

Setting  $V_1 = V_2$  yields:

$$\frac{R_T}{R_T + R_2} = \frac{R_A}{R_A + R_{SET}}$$

$$\frac{1}{1 + \frac{R_2}{R_T}} = \frac{1}{1 + \frac{R_{SET}}{R_A}}$$

$$\frac{R_2}{R_T} = \frac{R_{SET}}{R_A}$$

$$\frac{R_A}{R_T} = \frac{R_{SET}}{R_2}$$

From the given resistances  $R_2 = 2.2\ \text{k}\Omega$ ,  $R_{SET} = 3.3\ \text{k}\Omega$ ,

$$\frac{R_A}{R_T} = \frac{R_{SET}}{R_2} = \frac{3.3\text{k}}{2.2\text{k}} = \frac{3}{2} \quad R_A = \frac{3}{2} R_T$$

Looking up TDR's resistance from data sheet for  $-20^\circ\text{C}$ ,  $R_T = 920\ \Omega$ . So,

$$R_A = \frac{3}{2}(920) = 1380\ \Omega$$

